

2022-2023 Logic Circuits Final Exam

A combinational circuit that takes 2-bit signed 2's complement form A number (A_1A_0) and B number (B_1B_0) as input is requested to perform $C=A+B$ operation in signed 2's complement form at its output.

A	B	C
00	00	00
00	01	01
00	10	10
00	11	11
01	00	01
01	01	10
01	10	11
01	11	00
10	00	11
10	01	00
10	10	01
10	11	10
11	00	01
11	01	10
11	10	11
11	11	00

Q1: How many bits are required for output?
a) 2 b) 3 c) 4 d) 5

Q2: What is the logical expression of the least significant output?
a) $A_0 \oplus B_0$ b) $A_0 \oplus B_0$ c) $A_0 + B_0$ d) $A_0 \cdot B_0$

Q3: How many 2-input NAND gates can we achieve the least significant output with? (NOT including Gates will be)
a) 2 b) 3 c) 4 d) 5


Q4: We want to design a circuit with a minimum number of AND, OR, and NOT gates that will allow a 4-bit A number ($A_3A_2A_1A_0$) to output 1 if it is greater than 10 (10 in decimal system). What would be the logical expression of the output?
a) $A_3 + A_1$ b) $(A_3 + A_1) \cdot A_0$ c) $A_3A_2 + A_3A_1A_0$ d) $A_3A_2 + A_1 \cdot A_0$

A_3	A_2	A_1	A_0	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

Q5: X is a 3-bit number in 2's complement form. Our combinational circuit is required to perform $Z=X^2+2X+1$. How many bits must the Z output in 2's complement form be?
a) 4 b) 5 c) 6 d) 7

$$x = \begin{matrix} 2 & 1 & 0 \\ 0 & 1 & 1 \end{matrix} \quad x^2 + 2x + 1 = 8 + 3 + 1 = 13$$

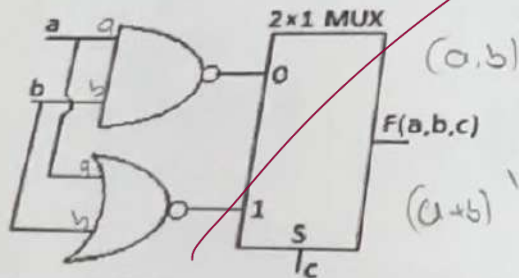
Q6: The minterms of the F output of the circuit below. What is the expression in terms of?
a) $\Sigma(2,4,6,7)$ b) $\Sigma(4,5,6,7)$ c) $\Sigma(1,3,5,6,7)$ d) $\Sigma(0,1,2,4)$



$$-16 \quad -13 = 10011$$

2's
0000
0001
0010
0011
0100
0101
0110
0111
1000
1001
1010
1011
1100
1101
1110
1111

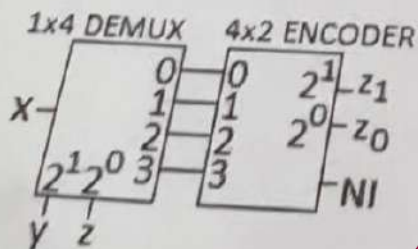Answer 3 questions according to the circuit below.
NOT: NI output 1 if no information comes to the inputs of the encoder and in this case the outputs z_1 and z_0 are unimportant.



Q7: What is the expression for the z_1 output?
a) x b) y c) z d) x'


Q8: What is the expression for the z_0 output?
a) x b) y c) z d) x'

Q9: What is the expression for the NI output?
a) x b) y c) z d) x'

Q10: A decoder circuit will be designed for the 7-segment display with common anode. Depending on the inputs (S_1 and S_0) of the decoder circuit, it is desired to display the numbers between 0 and 3. Based on this information, what would be the logical expression of the a segment output?


- $S_1 S_0 = 00$ ise ☐
- $S_1 S_0 = 01$ ise ☐
- $S_1 S_0 = 10$ ise ☐
- $S_1 S_0 = 11$ ise ☐

S_1	S_0	a
0	0	1
0	1	0
1	0	1
1	1	1

 

 - a) $S_1' \cdot S_0$ b) $S_1' + S_0$ c) $S_1 + S_0$ d) $S_1 + S_0$

The block representation of the full extractor is as follows. Accordingly, answer 2 questions.



Q11: What is the logical expression of debt output?

- a) $x' \cdot b_i + x' y + y \cdot b_i$ b) $x' y + b_i$ c) $(x \cdot y) b_i$ d) $x y b_i$

Q12: Complete extractor with decoder and OR gates we want to realize. How should we choose?

- a) 1 tane 2x4 decoder, 2 OR gate
- b) 1 tane 3x8 decoder, 2 OR gate
- c) 1 tane 2x4 decoder, 1 OR gate
- d) 2 tane 3x8 decoder, 1 OR gate

Q13: $f(a, b, c, d)$ prime implicants;

$c'd'$, ac' , $a'bd'$, $a'bc$ and then

Which of the following is not a essential prime implicants?

- a) $c'd'$ b) ac' c) $a'bd'$ d) $a'bc$

Q14: What would be the f output of the circuit below?

- a) $xy' + z$ b) $x' + y$ c) $x' yz$ d) $x' + y' + z'$

